

DESIGN OF ZIGBEE RF FRONT END IC IN 2.4 GHz ISM BAND

SUCHITAV KHADANGA

RFIC TECHNOLOGIES, BANGALORE, INDIA

<http://www.rficdesign.com>

Team-RV COLLEGE

Ashray V K	1RV12EC031
D V Raghu	1RV12EC050
Sanjith P Hemagiri	1RV12EC136
Rahul Verma	1RV13EC420

Outline

- **Introduction to ZigBee**
- **Objectives**
- **Motivation**
- **Block Diagram**
- **Specifications**
- **Methodology**

Introduction to ZigBee

- Based on IEEE 802.15.4 standard
- Supports 3 operating bands-
 - 868 MHz for Europe,
 - 915 MHz for US,
 - 2.4 GHz for the rest of the world
- IEEE 802.15.4 defines the radio physical and MAC layers whereas ZigBee defines the network, security and application frameworks for an IEEE 802.15.4-based system
- Suitable for simpler and less expensive wireless personal area networks

Objectives


To design, integrate and analyse the following components to fabricate a RF Front End IC for ZigBee applications in 180nm:

- Transmitter path consisting of the Power Amplifier (PA).
- Receiver path consisting of the Low Noise Amplifier (LNA).
- Switching circuitry to select transmit and receive paths.
- The associated matching networks.
- The harmonic filter.


Motivation

- Development of IoT: need for low cost and low power device for wireless communication
- Applications of ZigBee:
 - **Energy Management and Efficiency.**
 - **Home Automation.**
 - **Building Automation.**
 - **Industrial Automation.**
 - **Bio-Medical Applications.**

Methodology

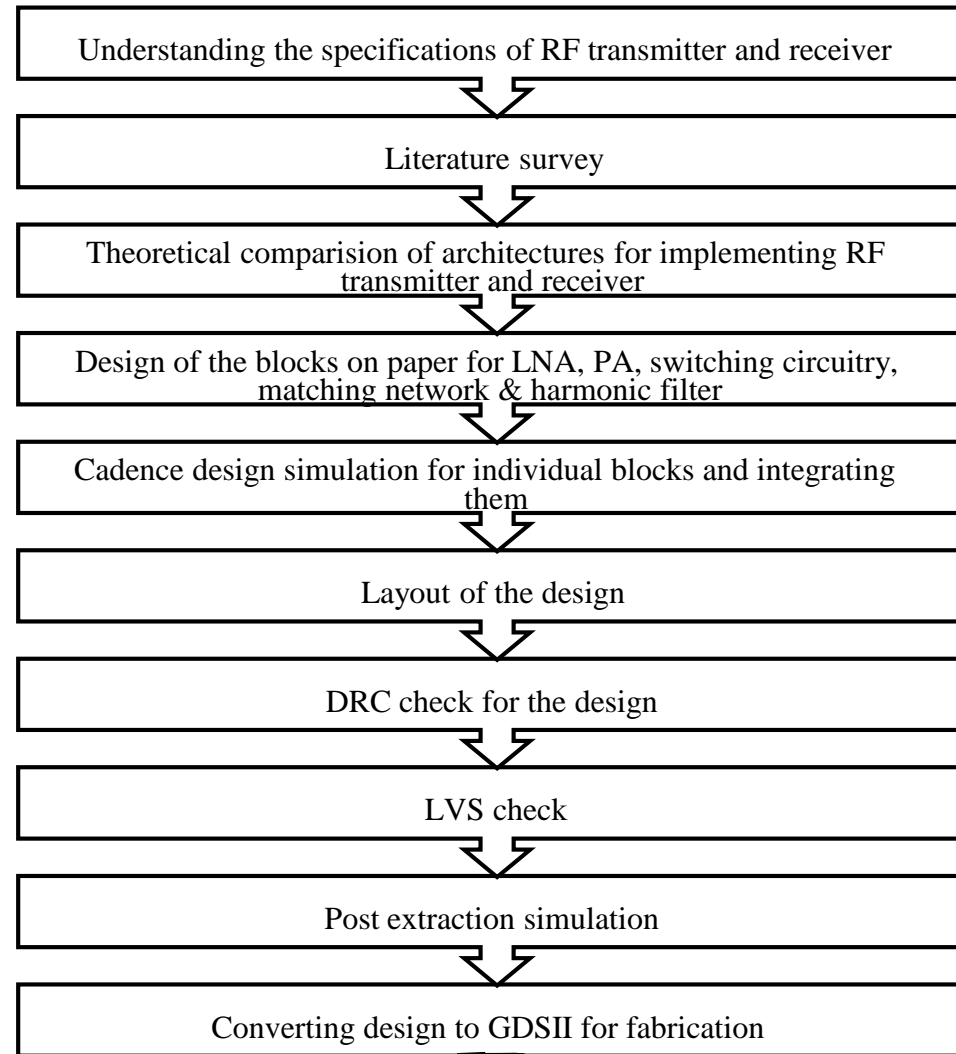

Block Diagram

 

Specifications

Transmitter Path Parameters

Supply Voltage	3.3 V
Operating Frequency Band	2.4 GHz to 2.5 GHz
Output P1dB	18 dBm
Saturated Output Power	20 dBm
Small Signal Gain	24 dB
Input/Output Impedance	50 ohm
TX Quiescent Current	18 mA
TX High Power Current	90 mA

Receiver Path Parameters

Supply Voltage	1.2 V
Operating Frequency Band	2.4 GHz to 2.5 GHz
Noise Figure	2.5 dB
Gain	12 dB
Input P1dB	-10 dBm
Input/Output Return loss	12 dB
RX Quiescent Current	10 mA
RF Port Impedance	50 ohm



Extra Information


Academic Pricing

Prototype Manufacturing Technology through CMC	Prices		
	Canadian Academic Peer-Reviewed Price	Canadian Academic Price	Note
Microelectronics	\$/mm ²	\$/mm ²	
STMicroelectronics 28nm CMOS FD SOI (through CMP)	\$4,000 See Fab Schedule To Apply	\$12,000 Apply Now!	Minimum charge is for a 1.25-mm ² design.
TSMC 65nm CMOS GP (through MOSIS)	\$2,250 See Fab Schedule To Apply	\$8,950 Apply Now!	Minimum charge is for a 1.1 x 1.1 mm ² design.
TSMC 65nm CMOS LP (through MOSIS)	N/A	Contact fab@cmc.ca .	
TSMC 90nm CMOS (through MOSIS): CRN90G	N/A	Contact fab@cmc.ca .	
GF (IBM) 0.13µm CMOS (through MOSIS): CMOSP13	\$800 See Fab Schedule To Apply	\$2,000 Apply Now!	Minimum charge is for a 1-mm ² design.
TSMC 0.18µm CMOS (through MOSIS): CMOSP18	\$800 See Fab Schedule To Apply	\$1,425 Apply Now!	Minimum charge is for a 1.1 x 1.1 mm ² design.
TSMC 0.35µm CMOS (through MOSIS): CMOSP35	\$200 See Fab Schedule To Apply	\$525 Apply Now!	Minimum charge is for a 1.1 x 1.1 mm ² design.
AMS 0.35µm CMOS - Standard (through CMP): AMSP35	\$225 See Fab Schedule To Apply	\$1,000 Apply Now!	
AMS 0.35µm CMOS - Opto (through CMP): AMSP35	\$225 See Fab Schedule To Apply	\$1,250 Apply Now!	

A 65-nm mask set can cost 1.8 times that of a 90-nm set, while a 45-nm mask set can cost 2.2 times that of a 65-nm set.

- EE Times 10/7/2010

CMOS RF INTEGRATED CIRCUITS


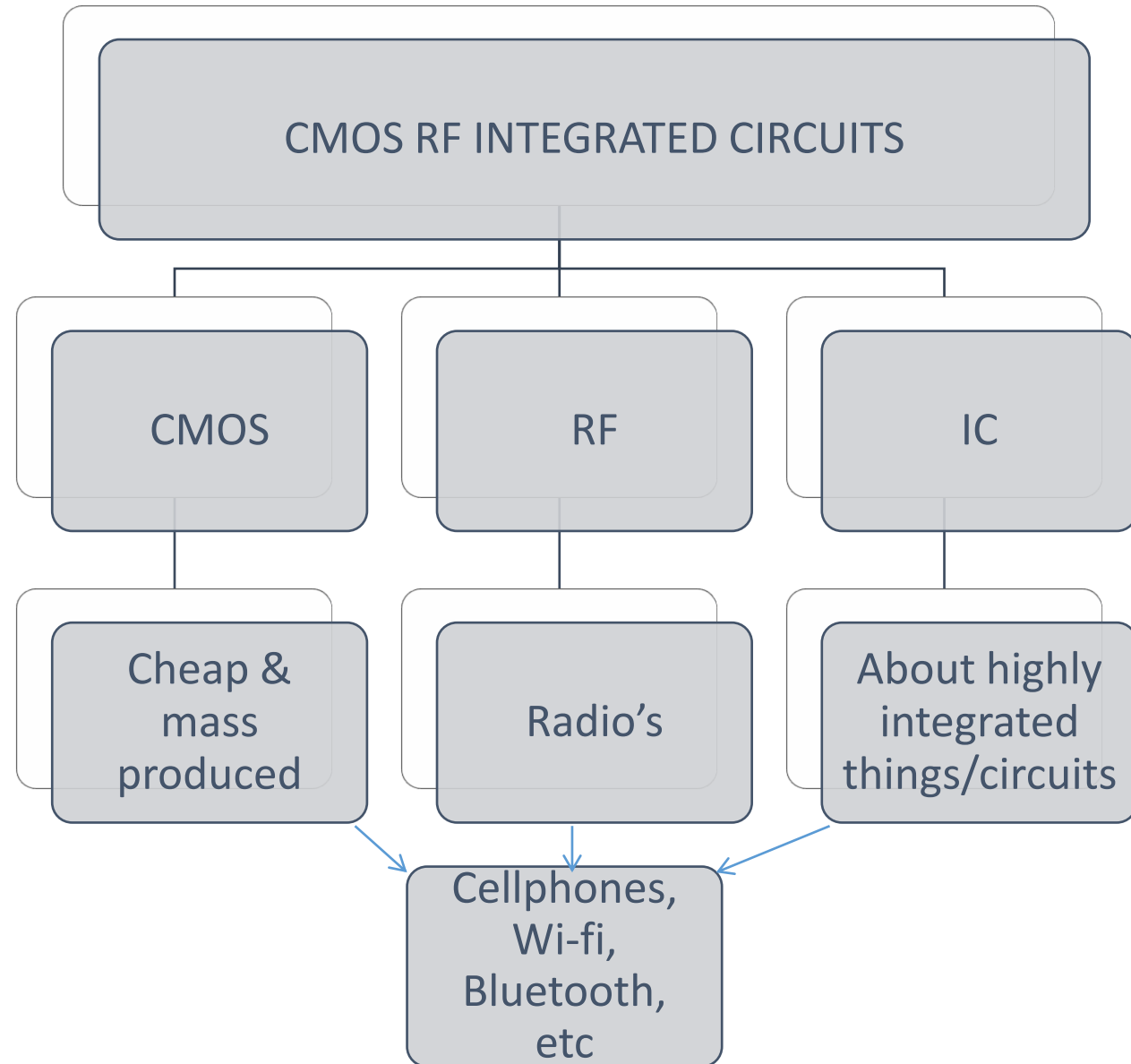


MOSFET



- Basic structure of MOSFET
- Formation of channel
- Different regions of operation: Cut-off, ohmic and saturation
- Final model of the MOSFET after considering all the capacitances- C_{gs} , C_{gd} , C_{gb} , C_{sb} , C_{db} ; gate resistance, contact resistance, inductance
- Metrics of MOSFET:

- Transition frequency,
$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

  - Max frequency,
$$f_{MAX} = \frac{1}{2} \frac{f_T}{\sqrt{2\pi \times f_T \times C_{gd}(R_g + R_s) + \frac{R_g + R_s}{r_o}}}$$




BASIC RF TRANSCEIVER

 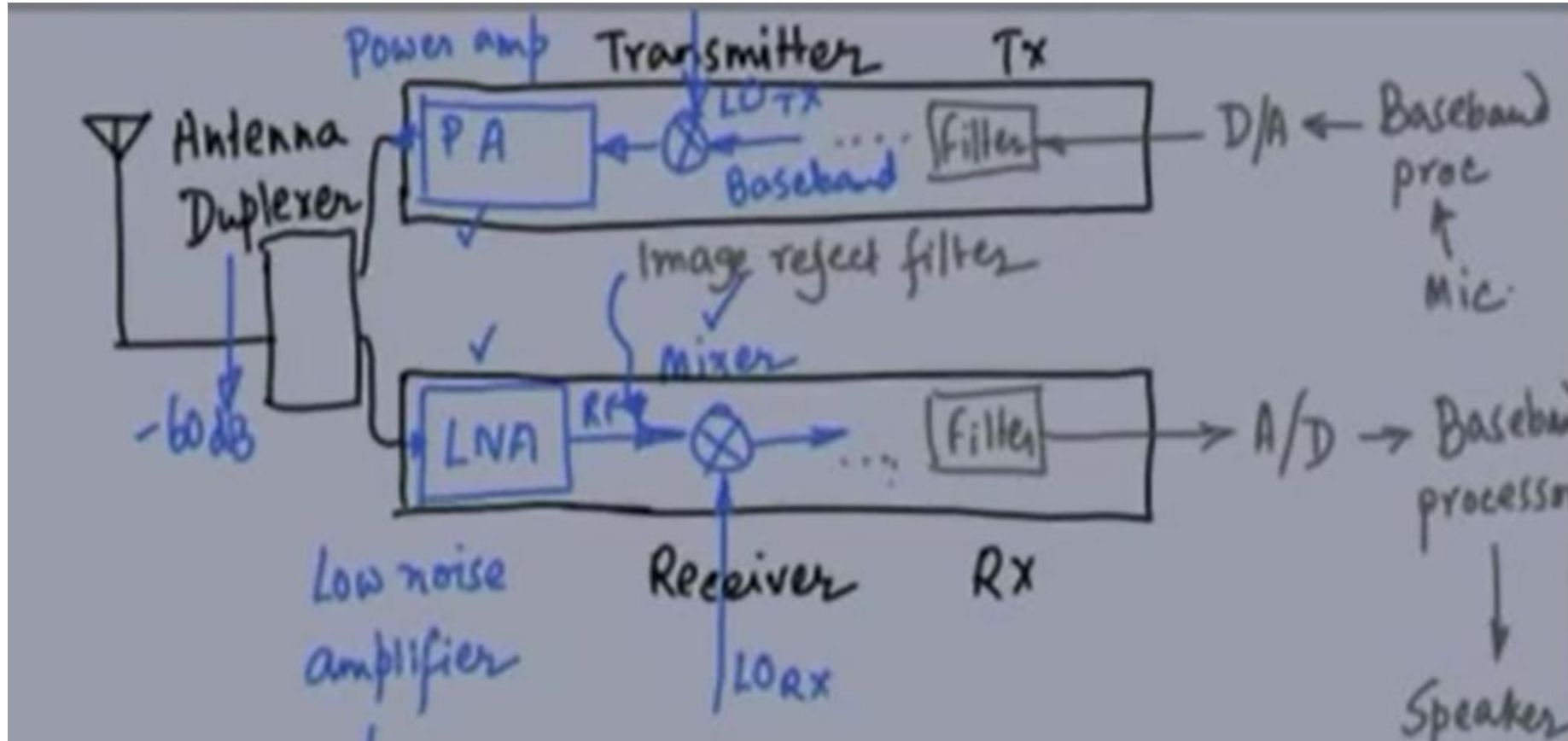

PRE-REQUISITES


- RLC
- Distributed Networks
- Elements of an IC
- MOSFETS

Reflection coefficient

 

$Z_S = Z_0 \rightarrow$ No echo's allowed


$Z_L = Z_0 \rightarrow$ No reflection

 

$Z_S = Z_0 = Z_L$

- Input of LNA has to be matched to Z_0 of antenna.
- Output of PA has to be matched to Z_0 of antenna.

TRANSMISSION MEDIA & REFLECTION

 



$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

Non conducting media $\rightarrow Z_0 = \sqrt{\mu/\epsilon} \approx \sqrt{\mu_0/\kappa\epsilon_0}$

Conducting medium $\rightarrow Z_0 \approx \sqrt{L'/C'}$

$L' \rightarrow$ inductance per meter
 $C' \rightarrow$ cap per meter

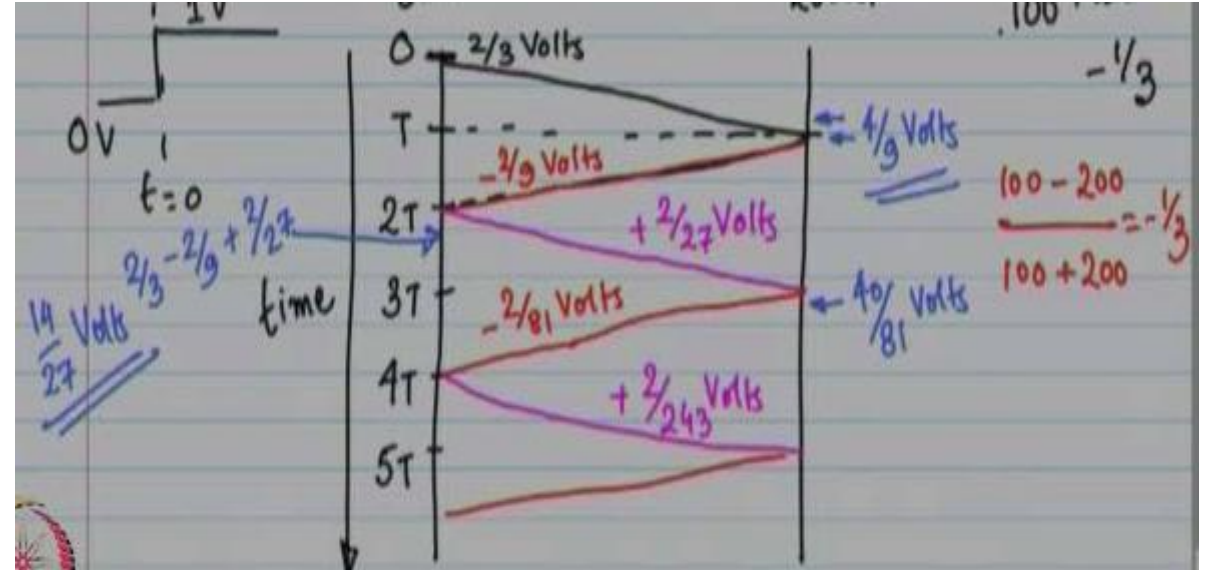
 
- When a wave is launched part of the energy is absorbed by load and part of it is reflected to source, at source, part of it is absorbed and remaining part is reflected back




- As time progresses to infinity, the voltage at source is equal to load and is equal to load to half.


➤ When load Z is equal to Z_0 then no reflection

  ➤ When load Z is not equal to Z_0 then no reflection



 


 - For no reflection:-
 - ❖ $Z_{LNAS} = Z_1 = Z_{MIXERL}$
- Typical value of characteristic impedance is:-
 - ❖ 75Ω – used for cable TV and all kind of T.V.
 - ❖ 50Ω – application other than T.V.



- For no reflection:-
 - ❖ $Z_s = Z_o$ of antenna

TRANSMISSION MEDIA & REFLECTION

 


- For no reflection:-

- $R_L = Z_0$

- $R_S = Z_0$

- $R_L = R_S = Z_0$

 


- To get maximum power received means –

- No reflection


- $P_{out} = P_{in} \times \text{Power Gain}$

- GSM phone has sensitivity of $-100\text{dBm} = 0.1\text{pW}$ which is extremely low. That's why maximum power transfer is important.

POWER GAIN

 

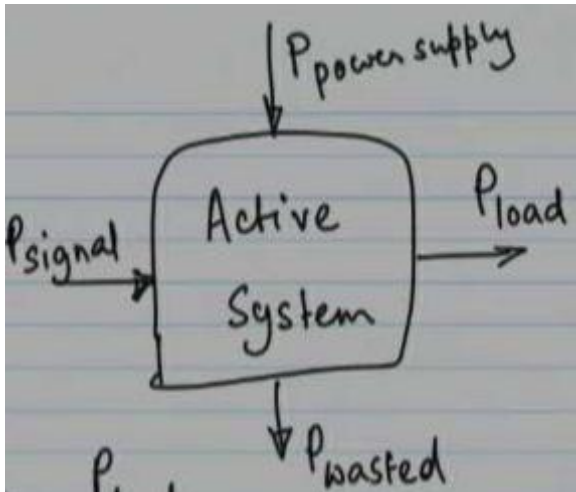
- Law of Conservation:
 - $P_{in} = P_{out} + P_{wasted}$
- Power Gain = P_{out}/P_{in}



- $P_{load} + P_{wasted} = P_{signal} + P_{power\ supply}$
- Quality Factor = $(w) \cdot (\text{Peak energy stored}) / (\text{average power consumed})$

RLC Network

Parallel RLC

 


$$I_L = \frac{IR}{jL/\sqrt{LC}}$$

$$I_C = jIR \cdot \frac{1}{\sqrt{LC}} \cdot C$$

$$|I_L| = |I_C| = I \left(\frac{R}{\sqrt{L/C}} \right)$$

Q

Series RLC

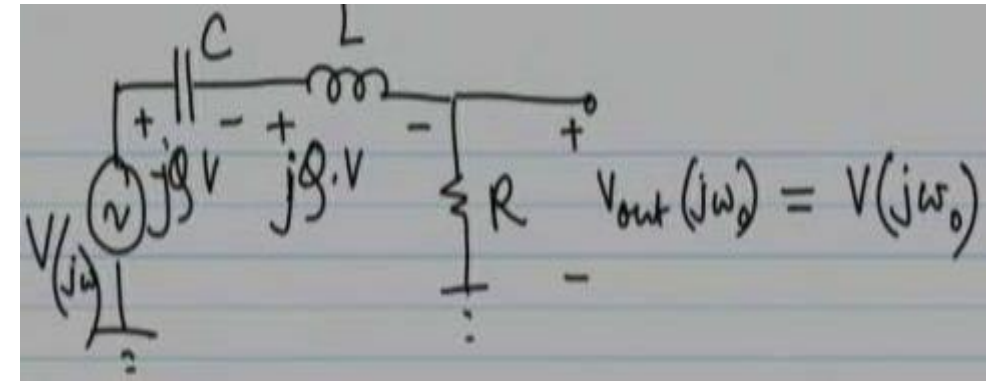


$$\frac{\sqrt{L/C}}{R}$$

Q

RLC Circuits


SERIES RLC
 
$$Q = \frac{1}{\omega_0 RC} = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$






PARALLEL RLC

$$Q = R \sqrt{\frac{C}{L}}$$

 

RLC Circuits

  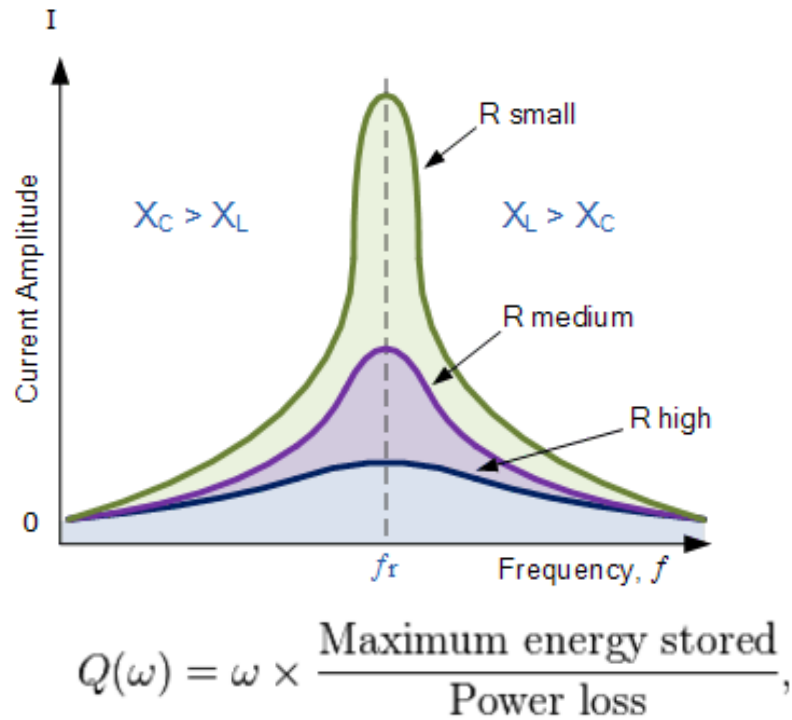

Transient Response of RLC Circuit for Step input



Example:

For GSM system, Center Frequency, ω_0 is 800MHz, channel spacing is 200KHz, calculate the Q factor. Is it possible to make an IC for the following system with the calculated Q?

$Q = (\omega_2 - \omega_1) / \omega_0$, $Q = 4000$. Not Possible, Since in an IC we can achieve maximum upto 10 or 15, above that we have to use discrete components to achieve max of 100.

RLC Circuits

SERIES RLC

 
 


$$R_p = R_s \left[1 + \left(\frac{\omega L_s}{R_s} \right)^2 \right] = R_s (1 + Q_s^2)$$

$$L_p = L_s \left[1 + \left(\frac{R_s}{\omega L_s} \right)^2 \right] = L_s \left(1 + \frac{1}{Q_s^2} \right)$$

Series-Parallel Transformation

PARALLEL RLC

  

$$R_p \approx Q_s^2 R_s$$

$$C_p \approx C_s.$$


$$R_p = (Q_s^2 + 1) R_s.$$

$$C_p = \frac{Q_s^2}{Q_s^2 + 1} C_s.$$

Matching Circuits

- Why do we need Matching ?

 - ☐ Retaining the shape of signal
- ☐ Maximum Power Transfer
- ☐ Avoid Reflections



$$Z_S = Z_L^*$$



Matching Circuits

- Matching Topologies:

- ☐ Transformer


- ❖ LC network

- ☐ L-Match

- ☐ π -Match

- ☐ T-Match


- ☐ Tapped L/C Match

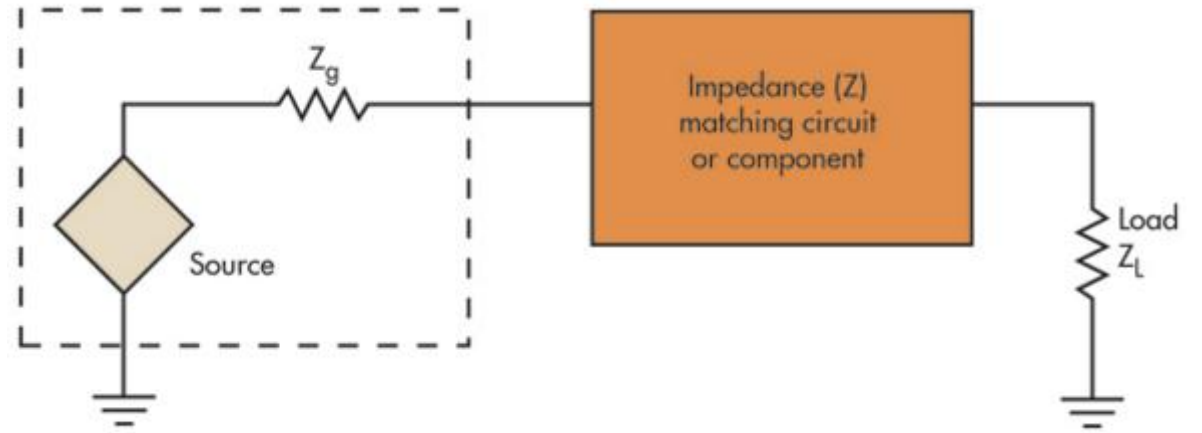

Matching Circuits

Transformer

 
- Ideal Transformers do not exist
- Its not lossless (Cu, Core)




$$N_s/N_p = \sqrt{Z_g/Z_L}$$

Matching Circuits


L-Match

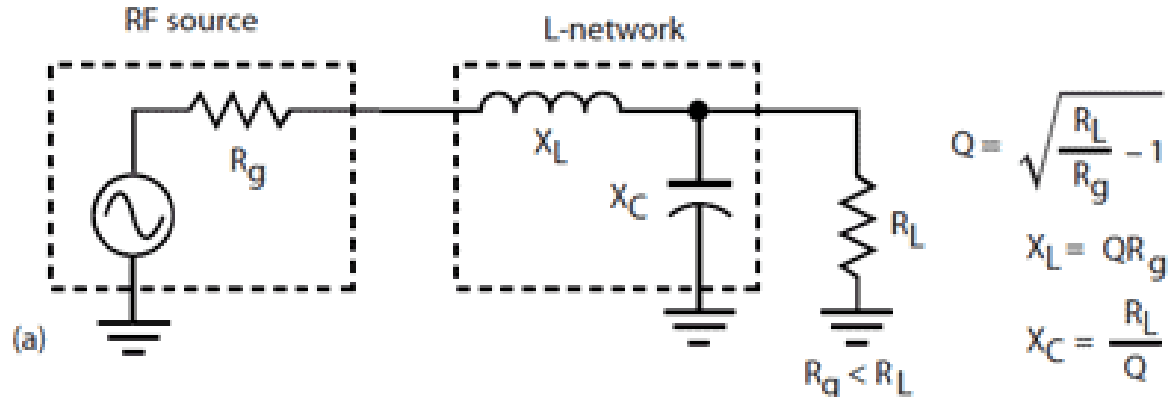


- Compute Q, L, C.

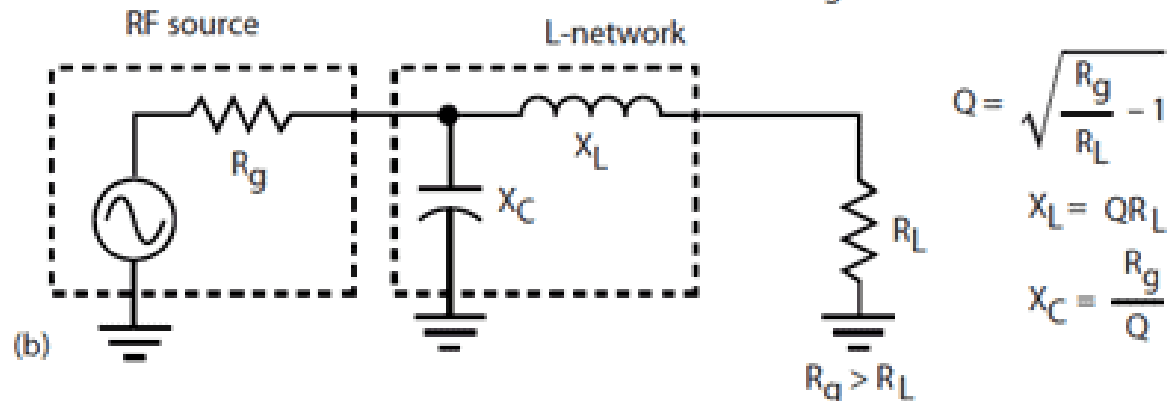

L-Match


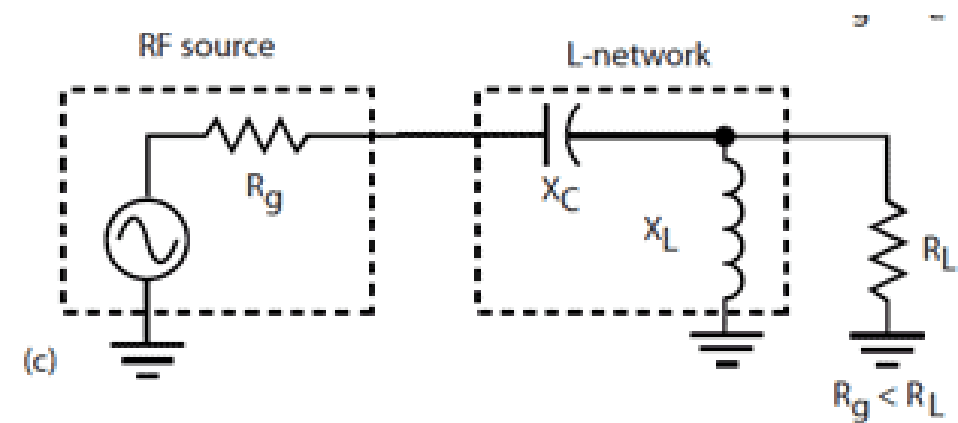


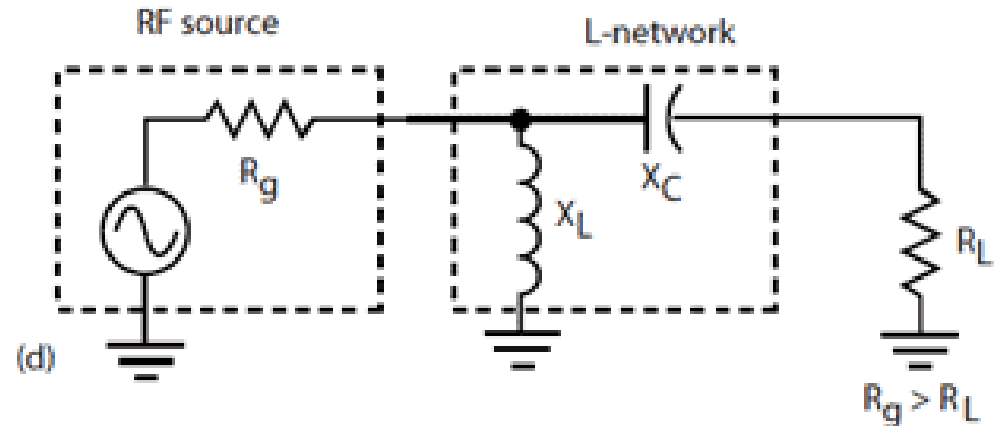- Only 2 Degrees of freedom, (L,C)
- Bandwidth limited due to Q





Other Matching Circuits

Π -Match

 
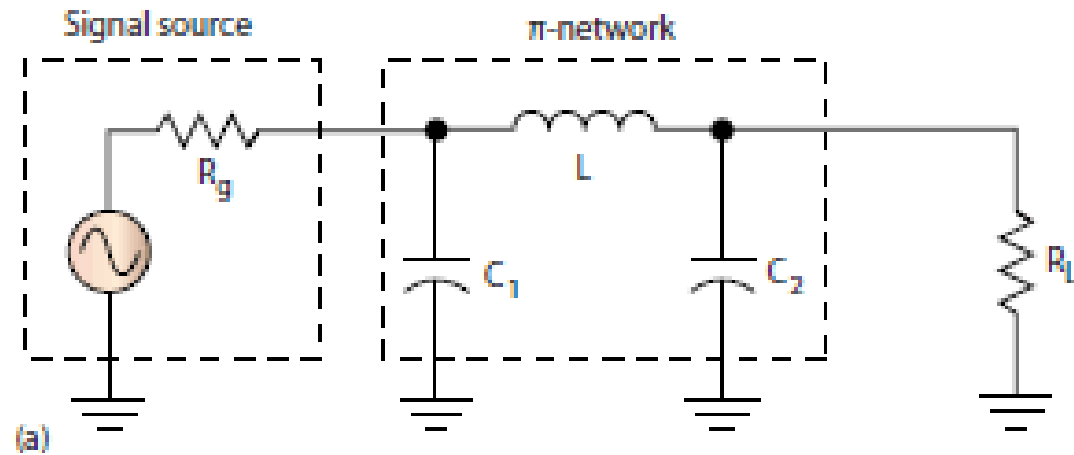


T-Match

  



Other Matching Circuits

Tapped L/C Match

  


Other Matching Circuits

Tapped L/C Match

  

Other Matching Circuits

- Comparison of Matching Networks

 

RESISTORS AND CAPACITORS

➤ **PASSIVE DEVICES** - does not need power supply


- Examples- R,L,C,M wires, diodes

➤ **ACTIVE DEVICES** – need power supply.

 - Examples- MOS,BJT,JFET etc.

$$A = w \cdot h$$



$$R = \rho l / A = (\rho / h) \cdot (l / w)$$



Resistors:



- made up of polysilicon or metal .

Capacitor

  

- Net capacitance, $C = A \epsilon / d + \text{fringing capacitance}$
- Fringing capacitance $\propto (\epsilon/d)$ (perimeter x height / fuzz factor)

Capacitor on IC:

  

- Area, Distance, Perimeter is important
- Fringing capacitance is important in normal capacitance when the distance between two plates is comparable than length a
- With MOSFET, well controlled, high density capacitance is achieved.

Passive IC Components: INDUCTORS

- Inductors resist change in magnetic flux thereby, induce an emf potential to oppose the change.
- Inductance depends on

$$L = \frac{1}{l} \mu_0 K N^2 A$$


- Non Idealities :

☐ Copper Losses

☐ Core Losses



Amount of power lost in Inductor : $i^2 \times R_{\text{copper}}$
 
$$R_{\text{copper}} = L \times \frac{\rho}{w}$$



Passive IC Components: INDUCTORS

  - Inductors resist change in magnetic flux thereby, induce an emf potential to oppose the change.



Inductors and Wires


Inductors

- Below resonant frequency, parallel LC N/W acts more like a inductor and above, it acts more like a capacitor
- While doing layout of the inductor
 - The top metal layer can be chosen to reduce the parasitic capacitance
 - The gap between the wires can be increased to reduce the turn-to-turn capacitance
 - The thickness of the wire can be increased to reduce the resistance of the wire
- To reduce Eddy currents
 - Can use the top most metal layer to increase the gap b/w inductor and substrate
 - Can use a more resistive substrate but is limited by the Latch-up problem. So use trenches and blocking mechanism to increase the resistivity

Inductors and Wires

Wires

 - Has resistance of $R = \frac{\rho * L}{\pi * R^2 - \pi * (R - d)^2}$ where skin depth, $d = \sqrt{\frac{2}{\mu * \sigma * \omega}}$
- Have Inductance per unit length of , $L' = \frac{\mu}{\pi} * \ln(h/r)$
- Observations:
 - Longer the wire, more the inductance
 - More the separation b/w the wire and substrate, more is the inductance of the wire



Wires

- Wire also has capacitance per unit length of $C' = \frac{w}{h} * \epsilon * (1 + \frac{1}{K})$

where K-fuzz factor



- Observations:

- As h increases. C' also increases, but L' decreases

- As w increases, C' also increases, but L' decreases

- Therefore, for any wire $L' * C' = \text{a constant}$

  - The model of the wire at RF frequencies is as shown:



Transmission Lines

- The characteristic impedance of the wire as a function of R' , L' , G' , C' and frequency is

$$Z_o = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

- If there exists reflections, then the shape of the input signal will be distorted as the signal takes time to settle to its final value.
- Voltage at any point on the wire is the sum of both the forward and backward moving wave
- The reflection coefficient at the load end is given by


$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o}$$

- Reflection coefficient is a function of frequency and hence, it is different for different frequencies

Low Noise Amplifiers

Motivation :

 - Noise of a system is greatly influenced by the first stage in a system.
- Increasing gain of the first stage also reduces the overall noise factor.
- Example :



- Nf of system is 2.4 when stage 1 has 10 dB as a gain
- Nf of system drops is 1.5 when stage 1 has 20db as a gain


Low Noise Amplifiers

- First stage in the receiver side needs to be an amplifier.
- From the previous study, the first stage needs to have low noise and high gain.
- Hence, the low noise amplifier.
- Requirements of a low noise amplifier :
 - ❖ Large Gain
 - ❖ Low noise figure
 - ❖ Linearity
 - ❖ Input and output Matching

Low Noise Amplifiers


Matching at input side :

Consider the following :

 

- Input at gate side of the Mosfet looks like a capacitor.
- One solution could be to add a resistor at the input, considering the matching network takes care of the capacitance.

Low Noise Amplifiers

 

Advantages


- ✓ Input matching is achieved.
- ✓ Good gain may be achieved.

Disadvantages

- Additional R_s contributes to additional noise.
- NF is atleast 2 , i.e greater than 3dB atleast.
- Thus, horrible NF even before considering the Mosfet.


Low Noise Amplifiers

Other possible design solutions:

 

Disadvantages :

 - 1) Channel noise adds up to the noise
- 2) Depends on g_m of the device.




Disadvantages :

Resistor is used here, and thus adds up to the noise. Use of resistors here is not recommended.



Still, used in some applications like oscilloscopes and active probes.

Low Noise Amplifiers

First cut design:

 


Analysing using small
signal model

  

$$Z'_m = Z + Z \cdot \frac{g_m}{j\omega C_{gs}} + \frac{1}{j\omega C_{gs}}$$

Low Noise Amplifiers

First cut design:

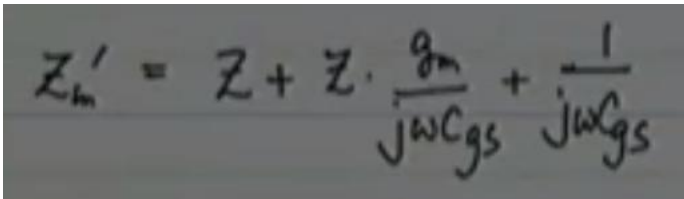 

$$Z'_{in} = Z + Z \cdot \frac{g_m}{j\omega C_{gs}} + \frac{1}{j\omega C_{gs}}$$

- Z cannot be a resistor, as we minimise use of resistors due to its contribution to noise.
- Z cannot be a capacitor as this will result in a negative resistance and would lead to positive feedback circuitry.
- Hence, using Z as an inductance would be a solution and Z_{in} would seem to have a resistive component of $g_m \cdot (L_s / C_{gs})$ which won't generate noise.
- When Z is used as inductance, the remaining L_s and C_{gs} can be tuned out with resonant frequency :

$$f_0 = \frac{1}{2\pi\sqrt{L_s \cdot C_{gs}}}$$

Low Noise Amplifiers

Load side:




- Gain here is approximately $\frac{\text{Load Impedance}}{\text{Degeneration Impedance}}$
- This gain might not be good enough.
- Also, C_{gd} here can cause instability.
- Hence, cascoded structure can be a good idea.

We also need to make sure that the first drain node needs to be a low impedance node since analysis of input side would change otherwise.

Low Noise Amplifiers


Load side:

 

- At this point too, impedance matching need to be done to get good gain.
- Impedance looking at load of M_2 should be same as impedance looking towards the source side of M_2
- This would then allow a proper matching to transfer the required power and get a desirable gain.

Low Noise Amplifiers


Load side:

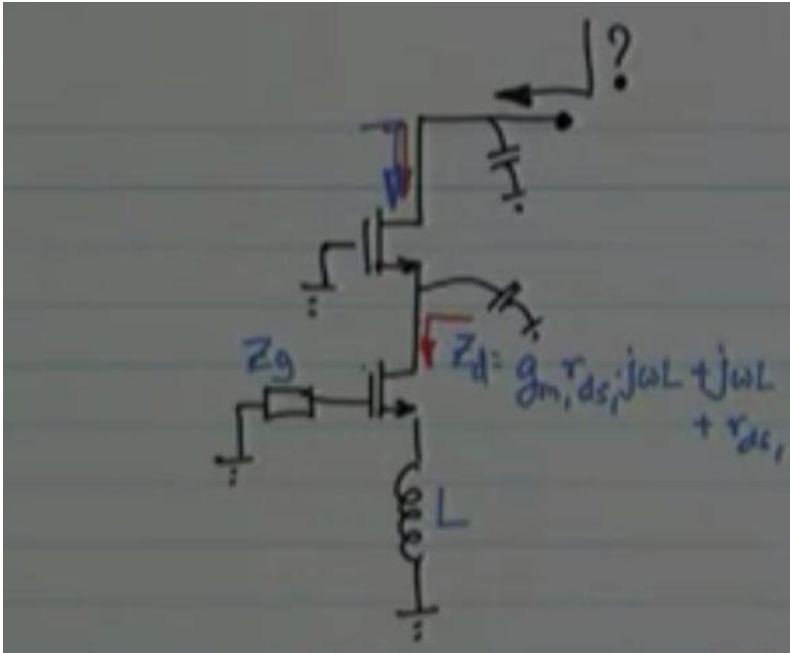

- Z_d is like a huge inductance.
- Thus, Z will finally look like large inductance.
- This will be able to drive load capacitances well.

Low Noise Amplifiers

FINAL LNA DESIGN

 

- Matching is achieved here.
- Decent gain is achieved due to cascade stage.
- Noise of the circuit depends on the channel noise of the first stage mosfet.
- The channel noise of the first mosfet depends on the C_{gs} of the device which in turn depends on the device geometry.
- Channel noise of the second mosfet doesn't play a significant role as it gets divided by the large gain.

Future work includes more insight into other topologies which includes noise cancellation techniques.

Power Amplifiers

➤ Important parameters of Power Amplifier-



➤ Efficiency

➤ Linearity

➤ Generic structure of Power Amplifier-

➤ Class A Power Amplifier

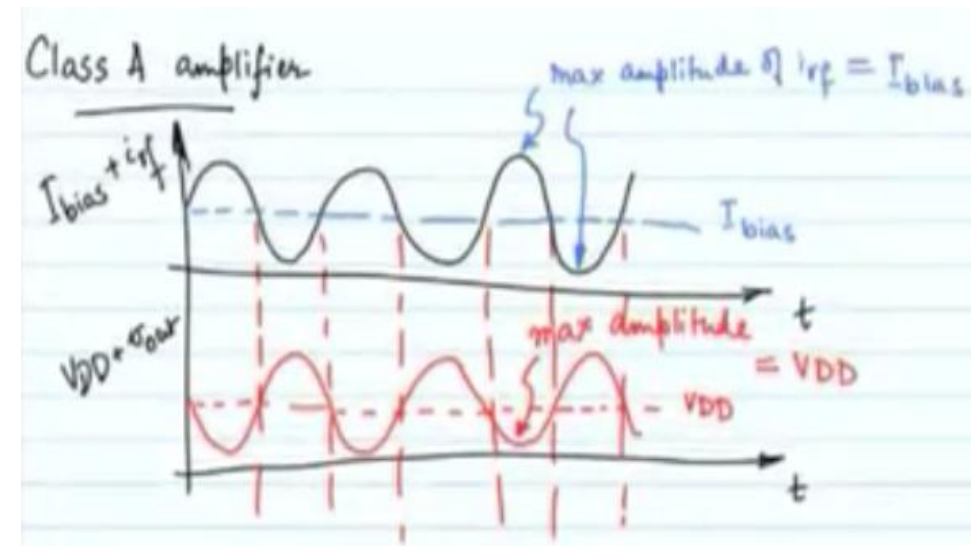
 
- Max Efficiency-50%
- Conduction Angle- 100%



Power Amplifiers

➤ Class B Power Amplifier

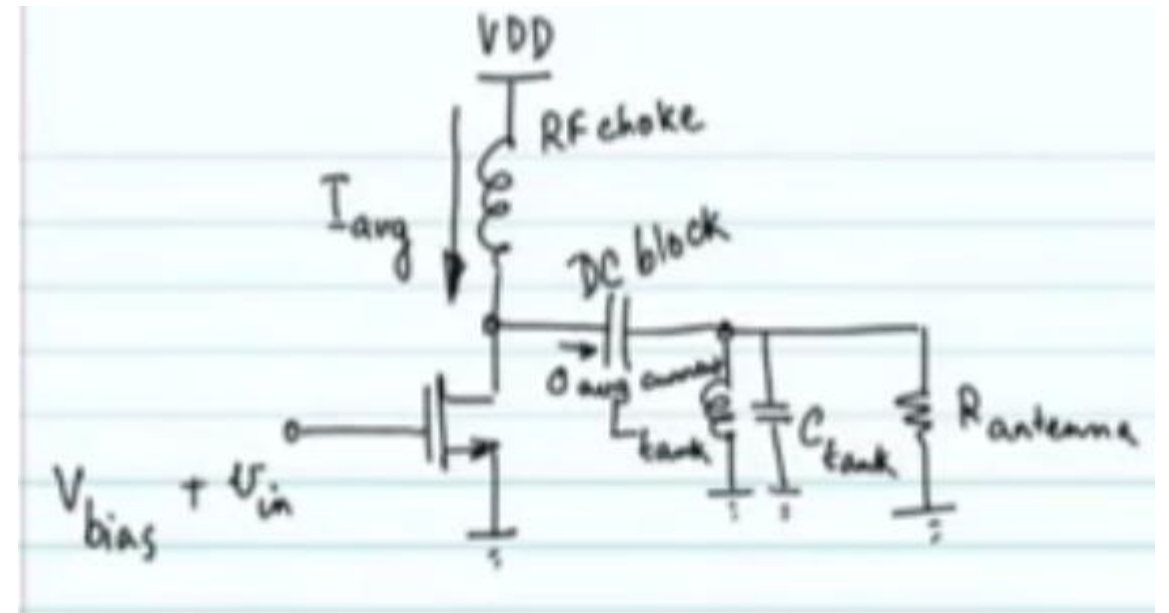
 
- Max Efficiency-78.5%
- Conduction Angle- 50%



Power Amplifiers

➤ Class C Power Amplifier

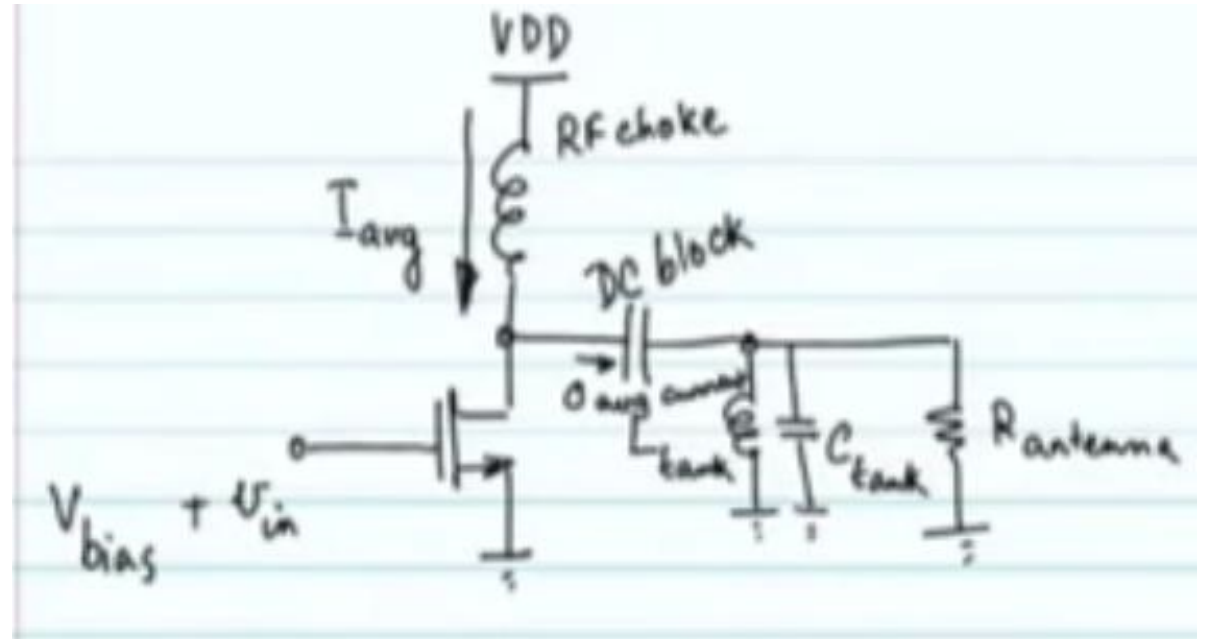 - Max Efficiency- $\eta = \frac{2*\phi - \sin(2*\phi)}{4*(\sin(\phi) - \phi*\cos(\phi))}$
- Conduction Angle- 50%



Valuable suggestions

Thank You